

Birla Institute of Technology and Science, Pilani
EEE C424 / INSTR C313 Microelectronic Circuits
Compre Exam I Semester 2012-2013

Max. Marks=2025

Time: 45 min.

Part A (open book)

Date: 12-12-2012

Note - Please note that there will be no partial Marking. Please write to the point answers.

Q1. What is input resistance R_{in} (looking into the gate) of a diode-connected MOS transistor. Now, what is output resistance R_{out} of this transistor with source degeneration resistor R_s ?



Ans. $R_{in} = 1/g_m$, $R_{out} = \frac{1}{g_m} + R_s$

Q2. When a common-drain stage is added between a common-source stage and a load resistor, what will be the effect on overall voltage gain and why?

Ans. Increase, CD stage isolates load resistor from CS stage and CD stage has low output resistance which increase drive capability and Gain increase.

Q3. Consider fig. Q3, Sketch and label I_x versus V_x as V_x varies from 0 to V_{dd} . Identify important transition points on the sketch.

Ans.

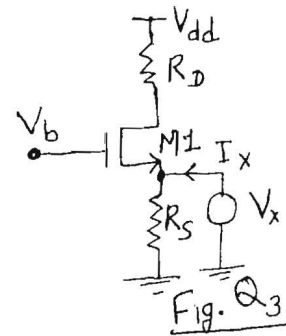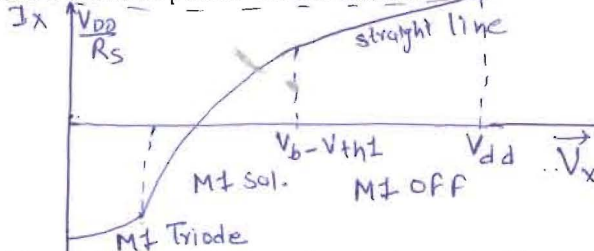

Q4. Consider a bias voltage generator circuit shown in Fig. Q4, Determine the value of V_2 and V_{dd}

required for this circuit to operate. Given: $\lambda_n = \lambda_p = 0$, $V_{sb} = 0$, $I_{bias} = 200 \mu A$,

$(W/L)_1 = 5$, $(W/L)_2 = 3$, $(W/L)_3 = 11$, $\mu_n C_{ox} = 140 \mu A/V^2$, $V_{tn} = 0.7 V$,


$\mu_p C_{ox} = 40 \mu A/V^2$, $V_{tp} = -0.8 V$

Ans.

$$V_1 = 0.7 + \sqrt{\frac{2 \times 200}{140} \times \frac{1}{5}} = 1.46 V$$

$$V_2 = 1.46 + \sqrt{\frac{2 \times 200}{140} \times \frac{1}{3}} = 3.136 V$$
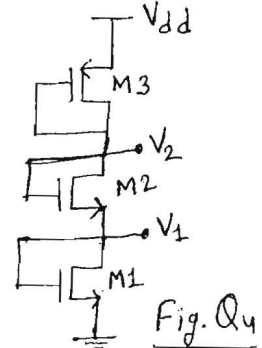
$$V_{dd} = 3.136 + \sqrt{\frac{2 \times 200}{40} \times \frac{1}{11}} = 4.89 V$$




Q5. Consider the circuit given in fig. Q5, If the overall capacitance at node V_{out} is dominated by $C_L = 1 pF$ and if $r_o = 200 k\Omega$ and $g_m = 600 \mu A/V$ for all transistors, Determine the value of R_{out} & hence ω_{-3dB} ?

Ans.

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \approx r_o/2 = 100 k\Omega$$
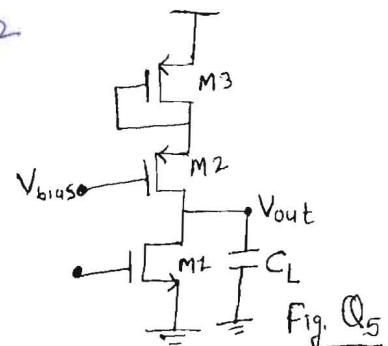
$$\omega_{-3dB} = \frac{2}{r_o C_L} \approx 10 Mrad/sec$$




Q6. Consider a circuit shown in Fig. Q6, Determine the value of R_E and hence find out the maximum value of R_C for the BJT to remain in the active mode. Given: $\beta = 100$, $V_{BE} = 0.7V$, $I_C = 2mA$, $V_{CE(SAT)} = 0.2V$.

Ans. $7.5 = 0.5k \times \frac{2m}{100} + 0.7 + (2m)R_E \Rightarrow R_E = 3.4k$

$$15 - R_C(2m) - 2m(3.4k) < 0.2$$


$$R_C \leq 4k$$

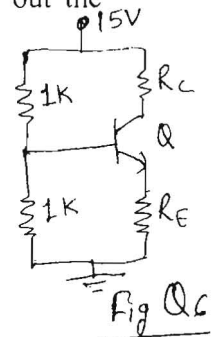

Q7. Identify type of feedback for circuit shown in Fig. Q7.

Ans.

Voltage sensing Current Mixing

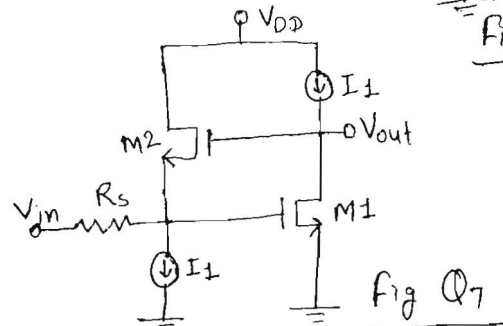


Q8. An amplifier having forward gain of 1000 and two poles at 1MHz and 10MHz. calculate the phase margin of a unity gain feedback amplifier.

$$P.M = 180^\circ - \left(\tan^{-1} \frac{100}{1} - \tan^{-1} \frac{10}{1} \right) = 6.28^\circ$$

$GBW = 100 MHz$

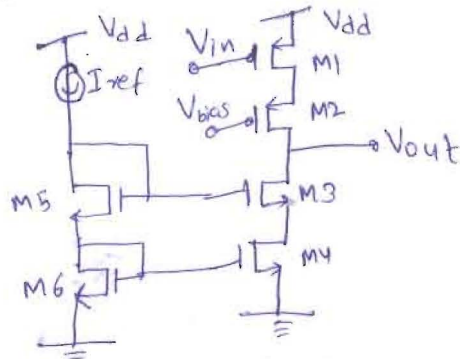Q9. Sketch and Label a pMOS cascode amplifier with a complete nMOS cascode current mirror load. Assume I_{ref} of the current mirror is ideal.



Q10. For the cascade amplifier of Question 9, Determine the value of overall output resistance R_{out} . Given $r_o = 200k\Omega$ and $g_m = 600\mu A/V$ for all transistors.

Ans.

$$R_{out} = r_o^2 g || r_o^2 g = \frac{1}{2} (200k)^2 (600\mu) = 12M\Omega$$

Q1 $\Rightarrow$ b) Poles $\rightarrow 4$

Solutions

c) $A_{v1} = -3.84 \text{ V/V}$
 $A_{v2} = -100 \text{ V/V}$

$\omega_3(I/P) = 8.8 \times 10^7 \text{ rad/sec}$

$\omega_2(O/P) = 4.5 \times 10^7 \text{ rad/sec}$

$\omega_L(\text{Intk}) = 2.09 \times 10^6 \text{ rad/sec}$

$\omega_H(\text{Att}) = 6.25 \times 10^{10} \text{ rad/sec}$

zeros $\rightarrow 3$


$\omega_{z1} = \omega_H/C_{gd} = 50 \times 10^9 \text{ rad/sec}$

$\omega_{z3} = \dots$

$\omega_{z2} = \omega_H/g_m = -2.5 \times 10^9 \text{ rad/sec}$

$A_v = 384$

$A_v = 51.6 \text{ dB}$


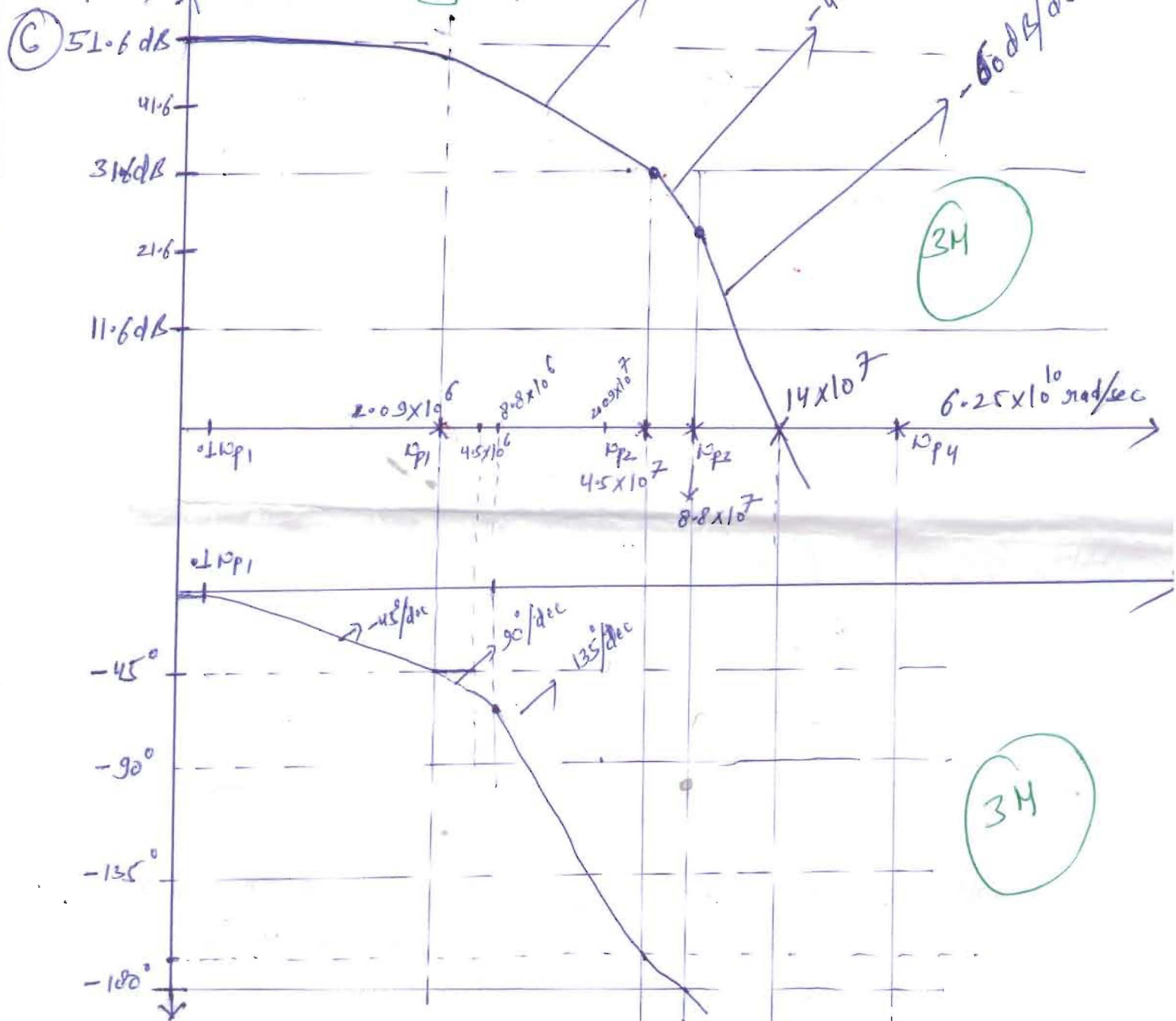


d) Phase Margin 0

e) Plot will remain same.

Q.2

(a) High freq. Small Signal Model.

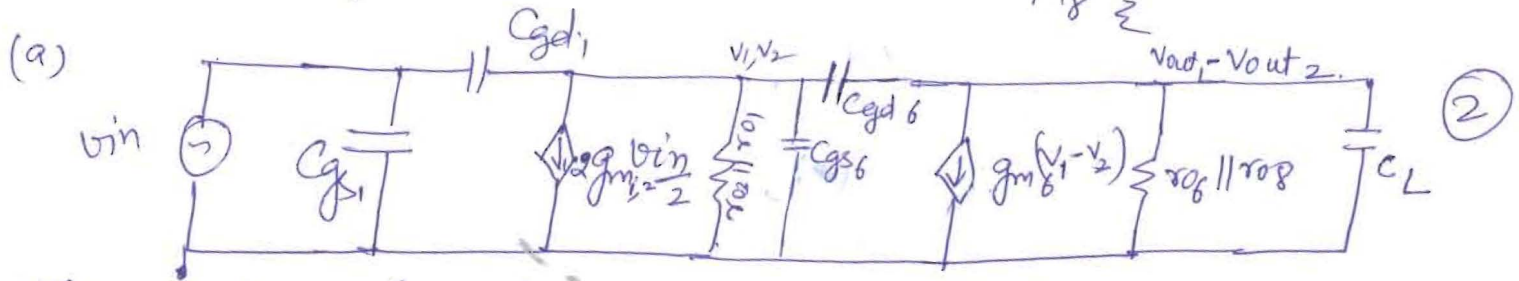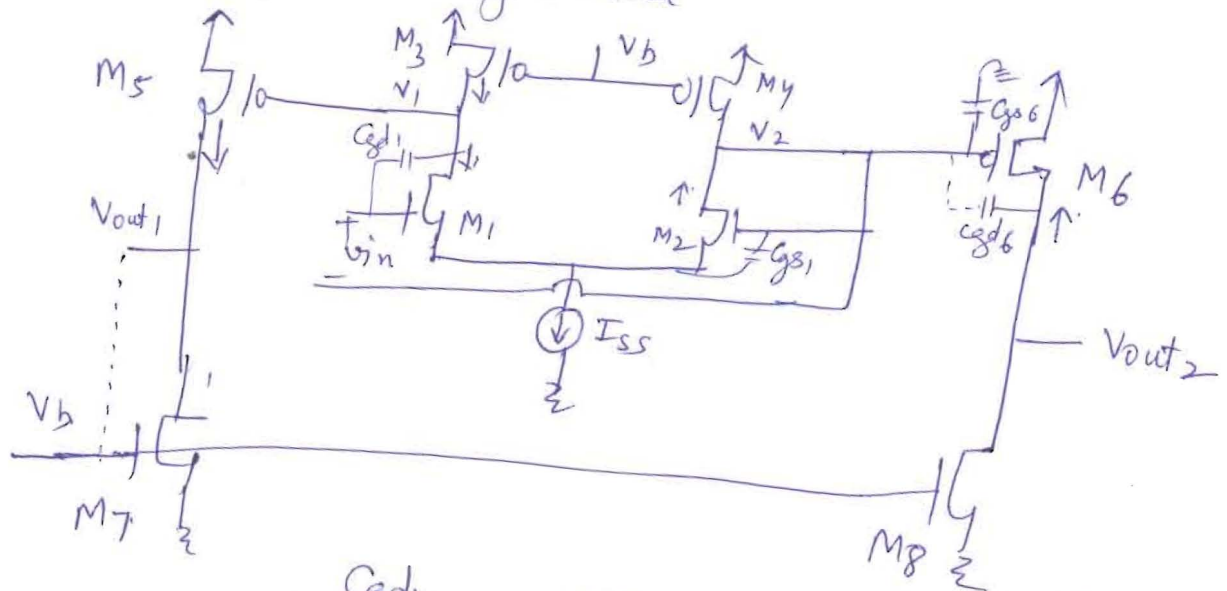

Without $V_{out1} - M_7$ Connection $\rightarrow$

(b) Low freq. small signal model. $A_0 = 2$
 $= + g_{m1}(r_{o1} || r_{o3}) g_{m6}(r_{o6} || r_{o8})$ (1)

(c) pole frequencies
 $\omega_{p1} = \text{nodes } v_1, v_2 \rightarrow \frac{1}{(r_{o1} || r_{o3})(C_{gs5} + C_{gd5} + \text{parasitic cap. } M_3, M_1, M_5)}$ (1)

$\omega_{p2} = \text{nodes } V_{out1}, V_{out2} \rightarrow \frac{1}{(r_{o6} || r_{o8})(C_L + \text{para. } q_{M_5, M_7})}$ (1)

transmission Zero freq.:-

$\omega_{z1} = \text{node } v_{in} \rightarrow + g_{m1}/C_{gd1}$ (12)

$\omega_{z2} = \text{node } V_{out1}, V_{out2} \rightarrow + g_{m6}/C_{gd6}$ (12)

(d) Transfer function $\rightarrow$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{A_0 (1 - \frac{s}{\omega_{z1}}) (1 - \frac{s}{\omega_{z2}})}{(1 + \frac{s}{\omega_{p1}}) (1 + \frac{s}{\omega_{p2}})} \quad (1)$$

With $V_{out1} - M_7$ Connection $\rightarrow$

(e) pole frequencies

node $v_1, v_2 = \omega_{p1} = \frac{1}{(r_{o1} || r_{o3})(C_{gs5} + \text{para. } q_{M_3, M_1, M_5})}$ (1)

pole frequency - ω_{p2} (node V_{out2}) $\approx - \frac{1}{(r_{o6} || r_{o8}) (C_L + \text{para. } g_{M6, M8})}$ (1)

pole freq. ω_{p3} (node V_{out1}) $\approx - \frac{1}{(\frac{1}{g_{m7}}) (C_{gs7} + g_{s8} + C_{gd5} + C_{db5})}$ (1)

Zero transmission frequency

ω_{z1} (node V_{in}) $\approx + g_{m1} / C_{gd1}$ (1)

ω_{z2} (node V_{out2}) $\approx + g_{m6} / C_{gd6}$ (1)

ω_{z3} (node V_{out1}) $\approx - \frac{2g_{m7}}{(C_L + C_{gs7} + g_{s8} + C_{db5} + C_{gd5})}$ (1)


(f) Transfer function

$$A(s) = \frac{V_{out2}(s)}{V_{in}(s)} \approx \frac{A_0 \left(1 - \frac{s}{\omega_{z1}}\right) \left(1 - \frac{s}{\omega_{z2}}\right) \left(1 + \frac{s}{2g_{m7} (C_L + C_{gs7} + g_{s8} + C_{gd5} + C_{db5})}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \left(1 + \frac{s}{\omega_{p3}}\right)}$$

$\downarrow$
 (1) $\left(1 + \frac{s (C_L + C_{gs7} + g_{s8})}{2g_{m7}}\right)$


Q3

Ans)

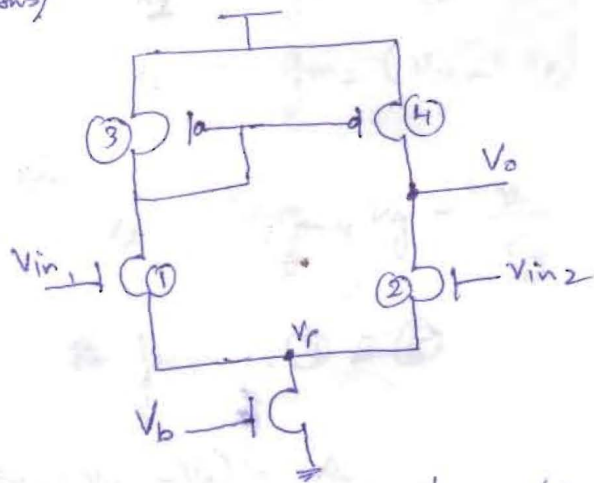Differential gain with $g_{m1} \neq g_{m2}$

$$V_{in1} - V_{in2} = V_{id}$$

$$V_{in1} = V_{id}/2 ; V_{in2} = -V_{id}/2$$

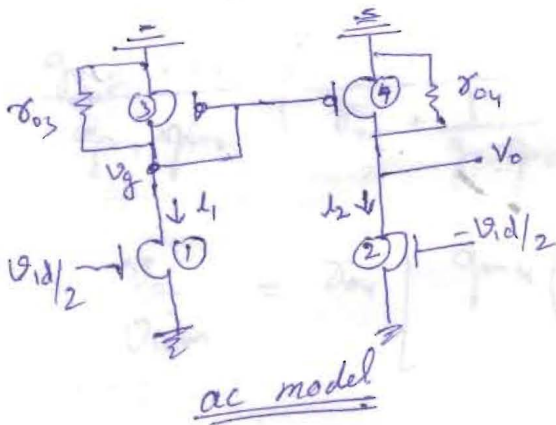ac model

$$I_1 = g_{m1} V_{id}/2 ; I_2 = g_{m2} (-V_{id}/2) \quad (1)$$

$$V_g = -I_1 \left(\frac{1}{g_{m3}} \parallel R_{o3} \right)$$

$$V_g = -g_{m1} \left(\frac{V_{id}}{2} \right) \left(\frac{1}{g_{m3}} \parallel R_{o3} \right) \quad (2)$$

Also,

$$I_2 = -g_{m4} V_g - \frac{V_o}{R_{o4}} \quad (3)$$

Equation (1) & (3)

$$-g_{m2} \frac{V_{id}}{2} = g_{m4} \left(g_{m1} \frac{V_{id}}{2} \right) \left(\frac{1}{g_{m3}} \parallel R_{o3} \right) - \frac{V_o}{R_{o4}}$$

$$A_{dm} = \frac{V_o}{V_{id}}$$

Solution Micro (Compre)

$$\frac{V_o}{R_{o4}} = g_{m4} \left(g_{m1} \frac{V_{id}}{2} \right) \left(\frac{1}{g_{m3}} \parallel R_{o3} \right) + g_{m2} \frac{V_{id}}{2}$$

$$\frac{V_o}{V_{id}} = \frac{R_{o4}}{2} \left[g_{m2} + g_{m1} g_{m4} \left(\frac{1}{g_{m3}} \parallel R_{o3} \right) \right]$$

$$\frac{V_o}{V_{id}} = \frac{R_{o4}}{2} \left[g_{m2} + g_{m1} \left(\frac{R_{o3}}{\frac{1}{g_{m3}} + R_{o3}} \right) \right]$$

$$\frac{V_o}{V_{id}} = \frac{R_{o4}}{2} \left[g_{m2} R_{o3} + g_{m1} R_{o3} \frac{g_{m2}}{g_{m3}} \right] \frac{1}{\frac{1}{g_{m3}} + R_{o3}}$$

$$\frac{1}{g_{m3}} \ll R_{o3}$$


$$\frac{V_o}{V_{id}} = \frac{(g_{m1} + g_{m2}) R_{o3}}{2} + \frac{g_{m2}}{2 g_{m3}} \quad (3)$$

Putting values of g_{m1} , g_{m2} , g_{m3} & R_{o3}

$$A_{dm} = \left(\frac{1.001 + 0.999}{2} \right) \frac{1000 \text{ k}\Omega}{2} + \frac{0.999}{2 \times 1} = 100.4995 \text{ V/V} \approx 40 \text{ dB} \quad (T)$$

Common-mode gain

$$V_{in1} = V_{in2} = V_{icm}$$

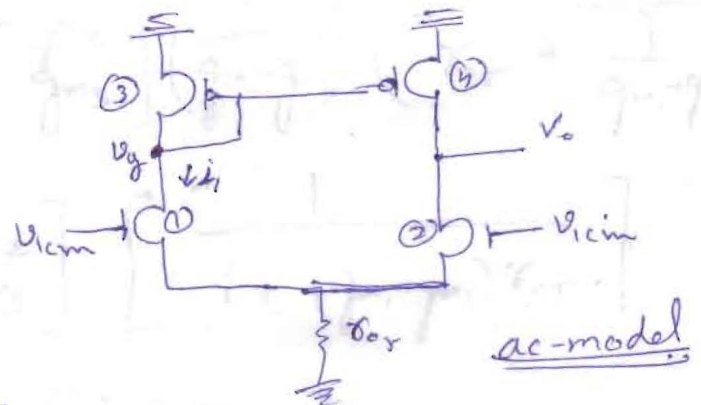ac-model

$$V_p = V_{icm} \frac{R_{o5}}{R_{o5} + \frac{1}{g_{m1} + g_{m2}}} \quad (1)$$

$$V_g = -I_1 \left(\frac{1}{g_{m3}} \parallel R_{o3} \right) \quad (2)$$

$$I_2 = g_{m1}(V_{icm} - V_P) \quad (3)$$

$$I_2 = g_{m2}(V_{icm} - V_P) \quad (4)$$

Also,

$$I_2 = -g_{m4}V_g - \frac{V_o}{\delta_{o4}} \quad (5)$$

from (4) & (5)

$$g_{m2}(V_{icm} - V_P) = -g_{m4}V_g - \frac{V_o}{\delta_{o4}}$$

$$g_{m2}\left(V_{icm} - \frac{V_{icm}\delta_{or}}{\delta_{os} + \frac{1}{g_{m1}+g_{m2}}}\right) = g_{m4}g_{m1}\left(V_{icm} - \frac{V_{icm}\delta_{or}}{\delta_{or} + \frac{1}{g_{m1}+g_{m2}}}\right)\left(\frac{1}{g_{m3}} \parallel \delta_{o3}\right) - \frac{V_o}{\delta_{o4}}$$

$$\frac{g_{m2}V_{icm}}{g_{m1}+g_{m2}}\left(\frac{1}{\delta_{os} + \frac{1}{g_{m1}+g_{m2}}}\right) = -\frac{V_o}{\delta_{o4}} + g_{m4}\left(\frac{1}{g_{m3}} \parallel \delta_{o3}\right)\left(\frac{g_{m1}V_{icm}}{g_{m1}+g_{m2}}\right)\left(\frac{1}{\delta_{or} + \frac{1}{g_{m1}+g_{m2}}}\right)$$

$$\frac{V_o}{V_{icm}} = \delta_{o4} \left[g_{m4}\left(\frac{1}{g_{m3}} \parallel \delta_{o3}\right)\left(\frac{g_{m1}}{g_{m1}+g_{m2}}\right)\left(\frac{1}{\delta_{or} + \frac{1}{g_{m1}+g_{m2}}}\right) - \frac{g_{m2}}{g_{m1}+g_{m2}}\left(\frac{1}{\delta_{or} + \frac{1}{g_{m1}+g_{m2}}}\right) \right]$$

$$\frac{V_o}{V_{icm}} = \delta_{o4} \left[\frac{\delta_{o3}}{\left(\frac{1}{g_{m3}} + \delta_{o3}\right)} g_{m1} - g_{m2} \right] \left(\frac{1}{g_{m1}+g_{m2}}\right) \left(\frac{1}{\delta_{os} + \frac{1}{g_{m1}+g_{m2}}}\right)$$

$$= \frac{\delta_{o4}}{\left(\frac{1}{g_{m3}} + \delta_{o3}\right)} \left[(g_{m1} - g_{m2})\delta_{o3} - \frac{g_{m2}}{g_{m3}} \right] \left(\frac{1}{g_{m1}+g_{m2}}\right) \left(\frac{1}{\delta_{os} + \frac{1}{g_{m1}+g_{m2}}}\right)$$

$$= \left[(g_{m1} - g_{m2})\delta_{o3} - \frac{g_{m2}}{g_{m3}} \right] \left[\frac{1}{1 + (g_{m1}+g_{m2})\delta_{os}} \right]$$

$$A_{cm} = \frac{(g_{m1} - g_{m2})\delta_{o3} - g_{m2}/g_{m3}}{1 + (g_{m1} + g_{m2})\delta_{os}}$$

(3)

Putting values of g_m 's & r_o 's


$$|A_{cm}| = 7.91 \times 10^{-3} \text{ V/V}$$

$$= -42 \text{ dB} \quad (1)$$

$$CMRR = \frac{r_{o3} \left(\frac{g_{m1} + g_{m2}}{2} \right) + \frac{g_{m2}}{2g_{m3}}}{\frac{(g_{m1} - g_{m2}) r_{o3} - g_{m2}/g_{m3}}{1 + (g_{m1} + g_{m3}) r_{o5}}} \quad (1)$$

$$= 81.95 \text{ dB} \quad (1)$$

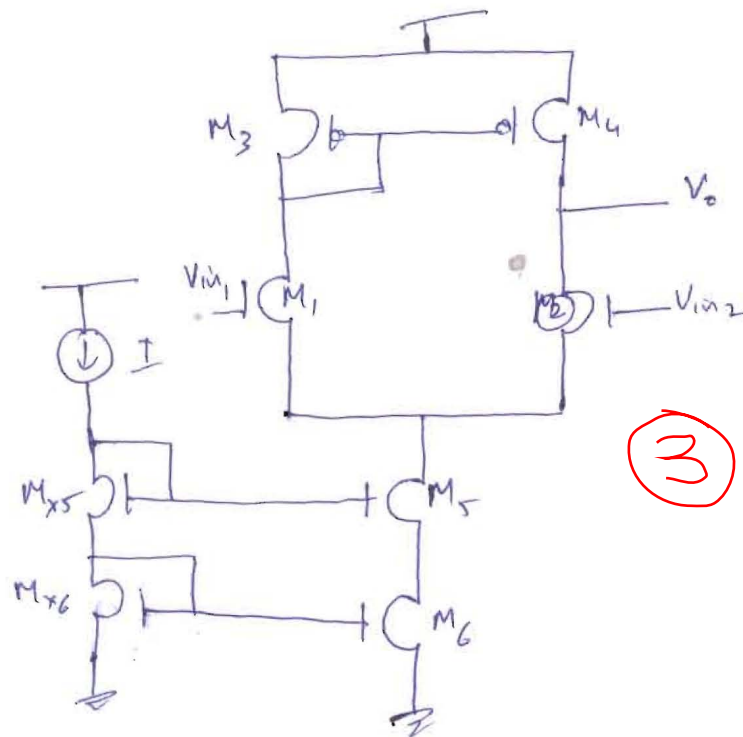b) To increase CMRR, one has to decrease A_{cm} .
 to decrease A_{cm} , one has to increase the tail resistance source. (2)



Q4

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_n |V_{ov,n}|^2$$

$$200 = \frac{1}{2} \times 140 \times 71.5 \times |V_{ov,n}|^2$$

$$|V_{ov,n}| = 0.2 \text{ V}$$

(1M)

Similarly,

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_p |V_{ov,p}|^2$$

$$200 = \frac{1}{2} \times 40 \times 250 \times |V_{ov,p}|^2$$

$$|V_{ov,p}| = 0.2 \text{ V}$$

(1M)

(1M)

$$g_{m1} = g_{m2} = g_{m3} = g_{m4} = \frac{2I_D}{V_{ov}} = 2 \text{ mA/V}$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = 25 \text{ K}\Omega$$

(1M)

$$(i) V_X = V_{in} - V_{GS4}$$

For M_1 to be in saturation:

$$V_{GS1} - V_{TH1} < V_{DS1}$$

or

$$V_{G1} - V_{TH1} < V_{D1}$$

$$(V_{in} - V_{GS4}) - V_{TH1} < V_{DD} - |V_{ov}/2| - |V_{ov}/3|$$

This condition may violate for max^m $V_{in} = V_{DD}$

ie.

$$(V_{DD} - V_{GS4}) - V_{TH1} < V_{DD} - |V_{ov}/2| - |V_{ov}/3|$$

$$or V_{GS4} + V_{TH1} > |V_{ov}/2| + |V_{ov}/3|$$

$$V_{GS4} > 0.2 + 0.2 - 0.3 = 0.1 \text{ V}$$

(3M)

(ii)

$$V_{out(max)} = V_{DD} - |V_{ov}/2| - |V_{ov}/3|$$

$$= 3.3 - 0.4 = 2.9 \text{ V}$$

$$V_{out(min)} = V_{OVCM1}$$

$$= 0.2 \text{ V}$$

(3M)

(iii) Max allowable dc voltage @ V_{in} (through M_1)

$$= V_{DD} - |V_{ov}/2| - |V_{ov}/3| - V_{TH1}$$

$$= 3.3 - 0.2 - 0.2 + 0.3$$

$$= 3.2 \text{ V}$$

other way, $V_{in} - V_{GS} = 2.9$
 $V_{DD} - 0.5 = 2.8$
 max allowable dc voltage @ V_X

$$= V_{DD} - |V_{ov}| = 3.3 - 0.2$$


$$= 3.1 \text{ V}$$

∴ max allowable dc voltage @ V_X

$$= 3.1 \text{ V} - 2.8 \text{ V}$$

(3M)

(iv)

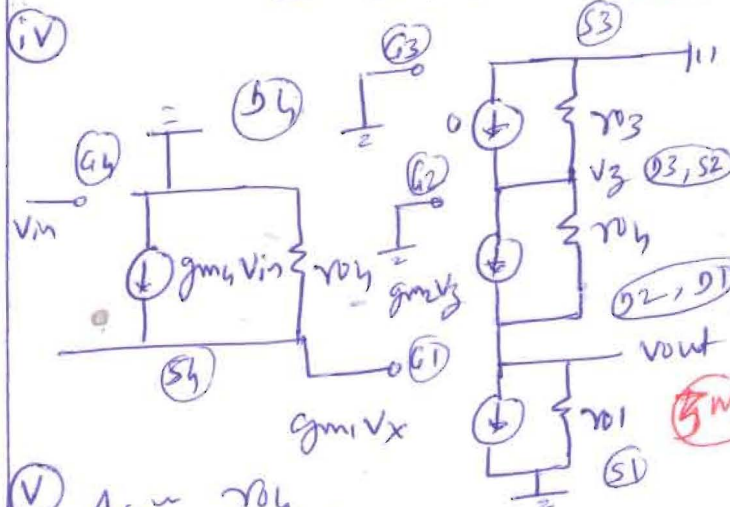

(v)

$$A_{v1} \approx \frac{r_{o4}}{r_{o4} + 1/g_{m4}} = \frac{25 \text{ K}\Omega}{25 \text{ K}\Omega + 500}$$

$$= 0.98 \text{ V/V}$$

$$A_{v2} \approx -g_{m2} [r_{o1} || g_{m2} r_{o2} r_{o3}]$$

$$\approx -2 \times [25 \text{ K}\Omega || 1250 \text{ K}\Omega]$$

$$\approx -2 \times 24.5 = -49 \text{ V/V}$$

$$A_v = A_{v1} \times A_{v2} = -48.03 \text{ V/V}$$

(4M)

Q5 (b)

at Q3.

$$100 \mu A = \frac{1}{2} \times 60 \frac{\mu A}{V} \times \left(\frac{40}{1}\right) \times (V_{GS} - 0.7)^2$$

$$V_{GS} = 0.99 \rightarrow V_{OV} = 0.29$$

$$V_2 = 2.5 - 0.29 = 2.21$$

at off.

$$1 \mu A = \frac{1}{2} \times 120 \frac{\mu A}{V} \times \left(\frac{20}{1}\right) \times V_{OV}^2$$

$$V_{OV} = 0.91 \rightarrow V_{GS} = V_{OV} + V_t = 1.61$$

$$V_{O2} = V_{GS} - V_{OV} = 0.99 - 0.91 = 0.08 \quad (\text{i.e. close to 0})$$

$$V_{O2} = \frac{V_2}{2.21} - \frac{V_{GS}}{1.61} = 0.6 \quad (\text{i.e. close to 1})$$

(1/2)

3

(a)

Q3 & Q4 form Current Multiplier.

$$\times \frac{120}{40} = \times 3$$

$$g_{m2} = g_{m1} = 2 \sqrt{\frac{1}{2} (120) \times \left(\frac{20}{1}\right) \times 100} = 693 \mu A/V$$

$$g_{m3} = 2 \sqrt{\frac{1}{2} \times 60 \times \left(\frac{40}{1}\right) \times 100} = 693 \mu A/V$$

$$g_{m4} = 2 \sqrt{\frac{1}{2} \times 60 \times \left(\frac{120}{1}\right) \times 100} = 2078 \mu A/V$$

$$g_{m5} = 2 \sqrt{\frac{1}{2} \times 60 \times \left(\frac{20}{1}\right) \times 1000} = 1550 \mu A/V$$

$$r_{o1} = r_{o2} = r_{o3} = \frac{24}{100} = 240 k\Omega$$

$$r_{o4} = 24/300 = 80 k\Omega$$

$$r_{o5} = 24/1000 = 24 k\Omega$$

2+3

(5)

(c) Open loop gain

$$A\beta \approx g_{m1} (r_{o1} || r_{o2})$$

$$[(3 \times g_{m1}) \left(\frac{r_{o4}}{3}\right)] \equiv g_{m1} \cdot r_{o1}$$

$$A\beta = 1$$

$$\therefore A = g_{m1} (r_{o2} || r_{o3})$$

$$A \approx 693 \times 120 \times 10^{-3} = 84$$

$$(d) A_f = \frac{A}{1 + A\beta} = \frac{84}{1 + 84 \times 1} = 0.9$$

$$R_o = r_{o5} || r_{o5} = 12 k\Omega$$

$$R_{of} = \frac{R_o}{1 + A\beta} = \frac{12 k\Omega}{1 + 84 \times 1} = 0.14$$

(e) To obtain $\frac{V_o}{V_s} = 5$. We could change direct connect from Q55 to Q26 by

Voltage Divider $\frac{R_1}{R_1 + R_2}$ to


change A from 1 to $\frac{1}{5.3}$ then.

$$A\beta = \frac{84}{1 + 84 \times \frac{1}{5.3}} = \frac{84}{16.8}$$

$$\text{New } 1 + A\beta = 16.8$$

$$R_{of}'' = \frac{R_o}{1 + A\beta} = \frac{12}{16.8}$$

$$= 0.714 \Omega$$

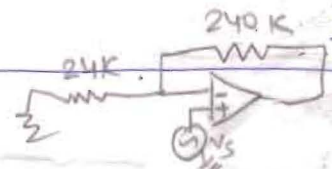

5) (b)

3. $100 \mu A = \frac{1}{2} \times 60 \frac{A}{V} \times \left(\frac{40}{1}\right) \times (V_{GS} - 0.7)^2$
 $V_{GS} = 0.99 \rightarrow V_{OV} = 0.29$
 $V_2 = 2.5 - 0.29 = 2.21$

4. $1 mA = \frac{1}{2} \times 120 \frac{A}{V} \times \left(\frac{20}{1}\right) \times V_{OV}^2$
 $V_{OV} = 0.91 \rightarrow V_{GS} = V_{OV} + V_t = 1.61$

$V_{O2} = V_{GS} - V_{OV} = 0.99 - 0.91 = 0.08$
 (i.e. less too)

$V_{O2} = 2.21 - 1.61 = 0.6$
 (i.e. less too)

Q3 & Q4 form Current Multiplier.

$\times \frac{120}{40} = \times 3$

$g_{m1} = 2 \sqrt{\frac{1}{2} (120) \times \left(\frac{20}{1}\right) \times 100} = 693 A/V$
 $= 2 \sqrt{\frac{1}{2} \times 60 \times \left(\frac{40}{1}\right) \times 100} = 693 A/V$
 $= 2 \sqrt{\frac{1}{2} \times 60 \times \left(\frac{120}{1}\right) \times 100} = 2078 A/V$
 $= 2 \sqrt{\frac{1}{2} \times 60 \times \left(\frac{20}{1}\right) \times 1000} = 1550 A/V$

$r_{o3} = \frac{24}{100} = 240 k\Omega$

$24/300 = 80 k\Omega$

$24/1000 = 24 k\Omega$

3+3

(c) Open loop gain

$A \beta \approx g_{m1} (r_{o1} \parallel r_{o3})$

$[(3 \times g_{m1}) \left(\frac{r_{o4}}{3}\right) \approx g_{m1} r_{o1}]$

$\beta = 1$

$\therefore A = g_{m1} (r_{o2} \parallel r_{o3})$

$A \approx 693 \times 120 \times 10^{-3} = 84$

(d) $A_f = \frac{A}{1 + A\beta} = \frac{84}{1 + 84 \times 1} = 0.988 \frac{V}{V}$

$R_o = r_{o5} \parallel r_{o5} = 12 k\Omega$

$R_{of} = \frac{R_o}{1 + A\beta} = \frac{12 k\Omega}{1 + 84 \times 1} = 140 \Omega$

(e) To obtain $\frac{V_o}{V_s} = 5$

We could change direct connection from Q55 to Q26 by

Voltage Divider $\frac{R_1}{R_1 + R_2}$ to

Change β from 1 to $\frac{1}{5.3}$

$A\beta = \frac{84}{1 + 84 \times \frac{1}{5.3}} = \frac{84}{16.8} = 5$

New $1 + A\beta = 16.8$

$R_{of}'' = \frac{R_o}{1 + A\beta} = \frac{12}{16.8} = 0.714 \Omega$

