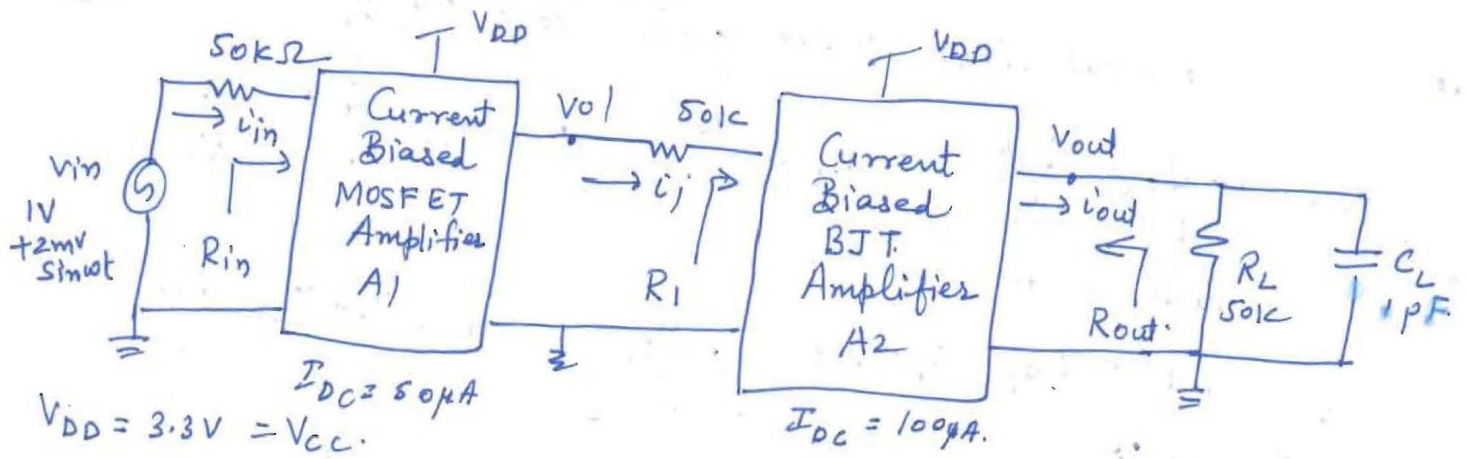


Part A CB

Q.

Sol.



$$V_{DD} = 3.3V = V_{CC}$$

$$I_{DC} = 50 \mu A$$

$$I_{DC} = 100 \mu A$$

$$\mu_n C_{ox} = 140 \mu A/V^2 \quad V_T = 0.7V, \quad \lambda = 0.1V^{-1}$$

$$\mu_p C_{ox} = 40 \mu A/V^2 \quad V_T = -0.7V, \quad \lambda = 0.1V^{-1}$$

$$V_{OV} = 0.2V$$

$$\beta = 100, \quad V_{CE,sat} = 0.2V, \quad V_A = 100V, \quad \frac{kT}{q} = 25mV, \quad I_S = 10^{-14}A$$

All Devices Biased in active region

(a) MOSFET

$$g_m = \frac{2I}{V_{OV}} = \frac{2 \times 50 \mu A}{0.2} = 0.5 \frac{mA}{V}, \quad r_o = \frac{1}{\lambda I} = \frac{1}{0.1 \times 50 \mu A} = 200 k\Omega$$

BJT

$$g_m = \frac{I_C}{V_T} = \frac{100 \mu A}{25mV} = 4 \frac{mA}{V}, \quad r_o = \frac{V_A}{I_C} = \frac{100V}{100 \mu A} = 1M\Omega, \quad r_{\pi} = \frac{V_T}{I_B} = \frac{25mV}{100 \mu A / 100} = 25 \Omega$$


$$V_{BE} = V_{Th} \ln \left(\frac{I_C}{I_S} \right) = 25mV \ln \left(\frac{50 \mu A}{10^{-14}} \right) = 25mV \ln [50 \times 10^8]$$

$$So, r_{\pi} = \frac{0.025}{0.558 \times 100} = \frac{2.5}{55.8} \times 10 = 0.558 k\Omega$$


(b)

Input Wave form w.r.t time.

$$V_{in} = 0.9V + 2mV \sin \omega t$$

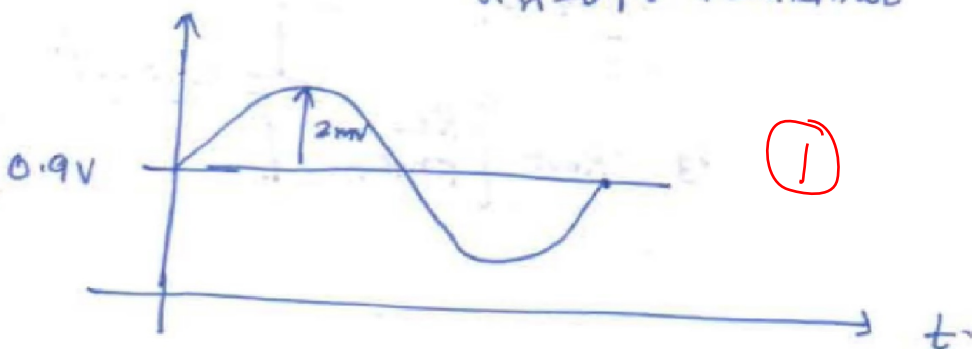

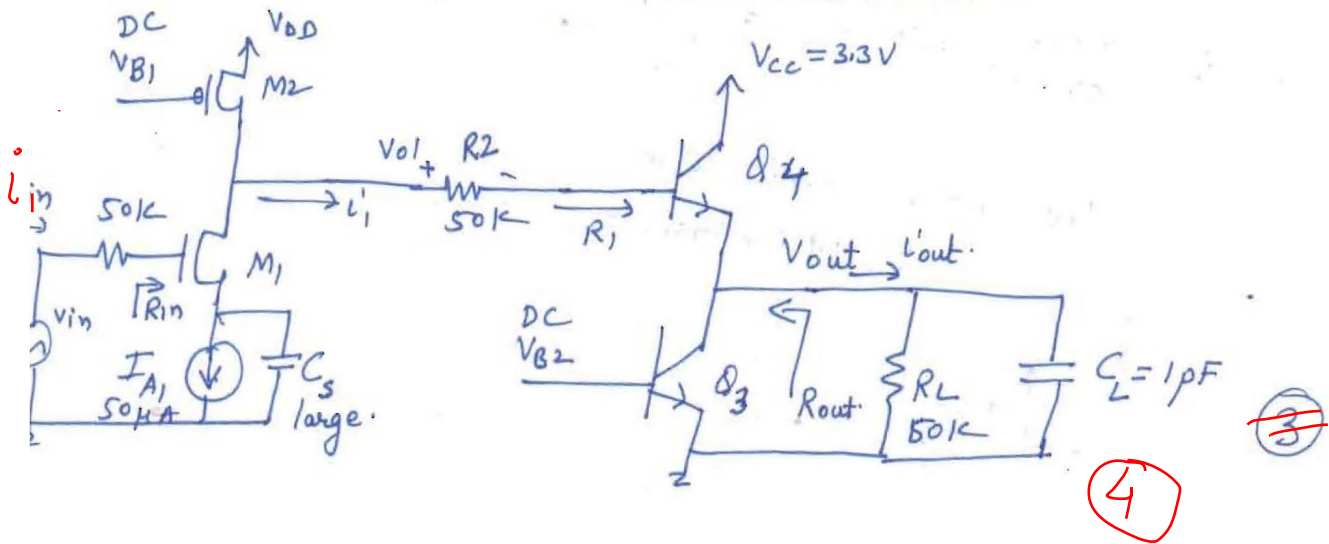(c) $A_1 \rightarrow \text{CSA}, A_2 = \text{Emitter Follower}$



(e) low frequency small signal voltage gain $A_v = V_{out}/V_{in}$ using $G_m R_{out}$

$$\frac{V_{out}}{V_{in}} = \frac{V'_{out}}{V_{in}} \times \frac{V_{out}}{V'_{out}} = G_m R_{out} \quad ; \quad G_m = \frac{V'_{out}}{V_{O1}} \times \frac{V_{O1}}{V_{in}}$$

$$V'_{out} = g_{m4} (V_{O1} - V_{out}) \quad , \quad V_{O1} = -g_{m1} (r_{o1} \parallel r_{o2}) V_{in}$$

$$V_{out} = V'_{out} (r_{o4} \parallel r_{o3})$$

$$\Rightarrow V'_{out} = g_{m4} (V_{O1} - V_{out} r_{o4/2})$$

$$\textcircled{2} \quad V'_{out} \left[1 + \frac{g_{m4} r_{o4}}{2} \right] = g_{m4} V_{O1}$$

$$\frac{V'_{out}}{V_{O1}} = \frac{g_{m4}}{1 + g_{m4} r_{o4/2}}$$

$$\text{Now } G_m = \frac{g_{m4}}{1 + \frac{g_{m4} r_{o4}}{2}} \times -g_{m1} (r_{o1/2}) = \frac{-g_{m1} g_{m4} (r_{o1/2})}{(1 + \frac{g_{m4} r_{o4}}{2})}$$

$$= \frac{0.5 \text{ mA/V} \times 4 \text{ mA/V} (0.1 \text{ M})}{(1 + 4 \text{ m} \times 1 \text{ M}/2)} = \frac{0.2}{1.5} \text{ A/V}$$


(d)

$$R_1 = r_{\pi} + (\beta + 1)(r_{o3} \parallel R_L)$$

≈ 25
 $558 \text{ k}\Omega + (100) \parallel 0.5 \text{ M}\Omega$

$$R_1 \approx 100 \text{ M}\Omega$$

$$50 \text{ M}\Omega$$

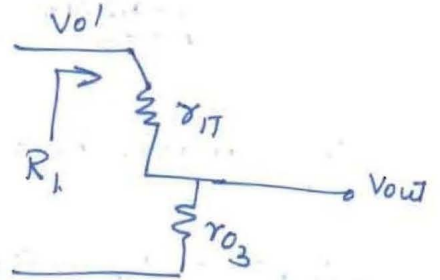


DC power dissipated = $V_{dd} (50 + 100) \mu\text{A}$
= 0.495 mW

with $I_{ref} \Rightarrow \text{DC Power} = 0.98 \text{ mW}$

$\textcircled{1}$

A_1 is single output differential amplifiers & A_2 is common base amplifier
($V_{id} = V_{in}$)

(f)

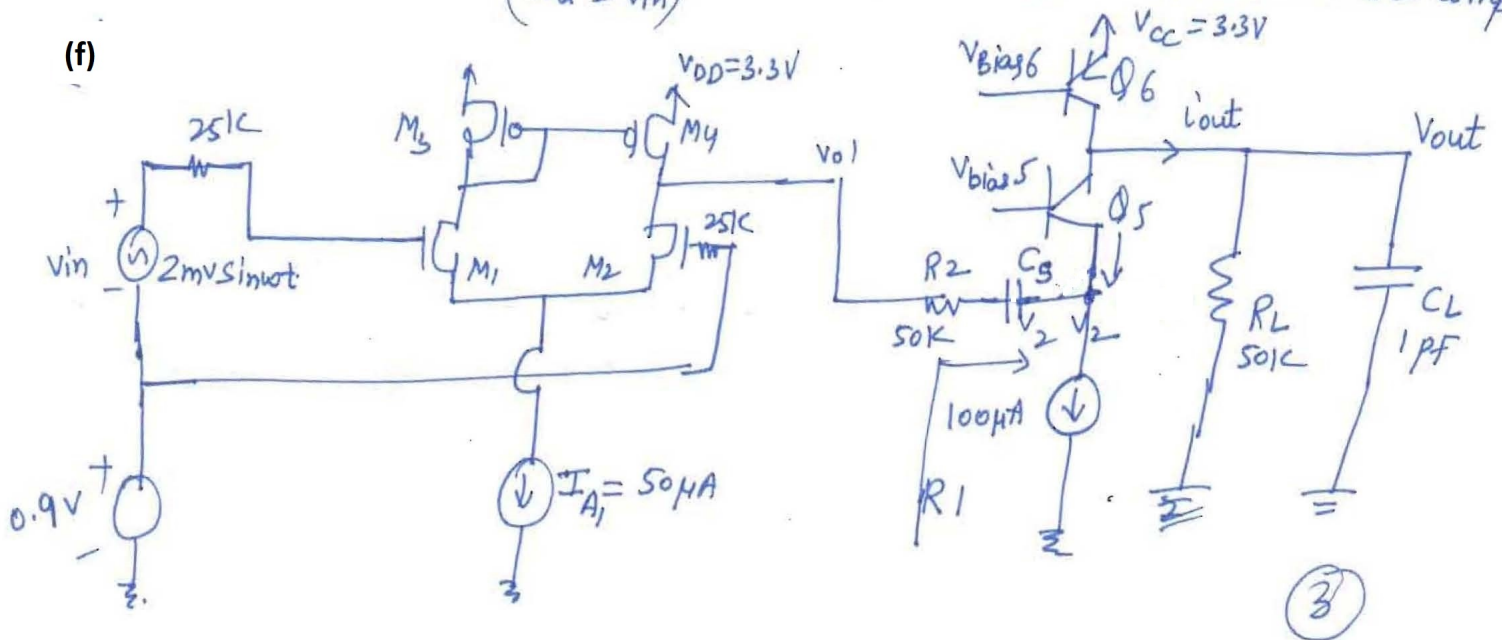

(g)

$$A_{cm} = \frac{V_{out}}{V_{icm}} = \frac{1}{1 + 2g_m R_{ss}} = 0.01 \quad \textcircled{1}$$

$$R_{ss} = 100 \text{ K}, g_m = 0.5 \text{ mA/V}$$

for perfect matching (

$$\begin{aligned} |A_{dm}| &= g_{m1} (r_{o1} || r_{o2}) || \frac{1}{g_{m5}} \\ &= \frac{1}{2} \frac{\text{mA}}{\text{V}} \times \frac{0.1 \text{ M}\Omega}{250} \\ &= \frac{1}{2} \text{ mA} \times \frac{100 \text{ K}}{250} \\ &= \frac{50}{125} \end{aligned}$$

$$g_{m5} = 4 \frac{\text{mA}}{\text{V}}$$

①

(h)

$$0.83 \text{ mV}$$

$$|V_{offset}| = \frac{V_{o1}}{A_{dm}} = \frac{V_{o1}}{\frac{50}{125}} = \frac{0.1 \text{ mV}}{50} = 0.002 \text{ mV} = 2 \mu\text{V}$$

①

Q2


stage-1

(a)

cascode

Common Gate amplifier,

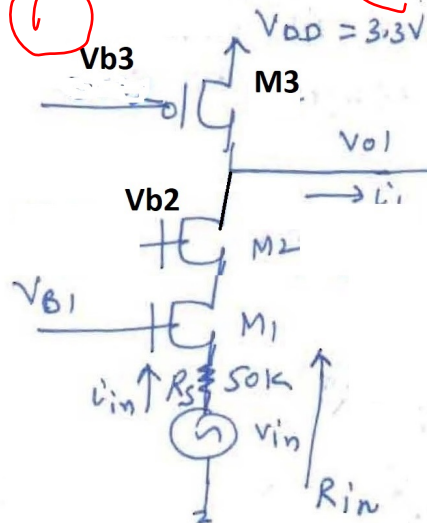
o/p Swing $\rightarrow (3.3 - 0.2) - (0.2)$



Stage-2

Common Emitter Amp.

~~with cascode load~~

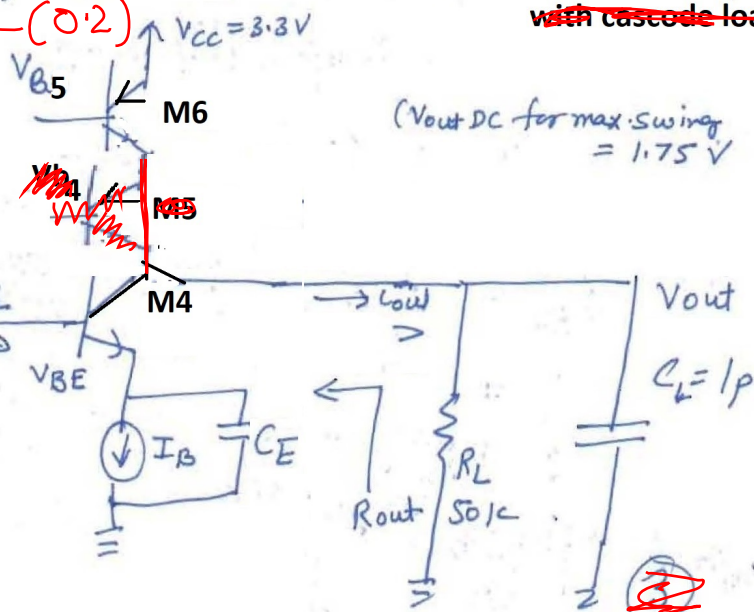

(b)

$$R_{in} = \frac{R_L + r_{o1}}{1 + g_{m1} r_{o1}} = \frac{r_{o2} + r_{o1}}{1 + g_{m1} r_{o1}} = \frac{(0.2 + 0.2) \text{ M}\Omega}{1 + 500 \mu \times 0.2 \text{ M}} = \frac{0.4 \text{ M}}{101} = 3.96 \text{ k}\Omega \approx 4 \text{ k}\Omega$$

$$= 2/g_m \approx 4k$$

(c)

$$V_{out} = i_{out} (50k \parallel 100k) \approx i_{out} 50k = -50 \text{ mV} \quad 150 \text{ mV}$$



$$i_{out} = -\beta i_1 = -100 \times 0.029 = -2.9 \mu A$$

$$i_1 = \frac{200k}{200k + (50k + 558k)} i_{in} = 0.01 \mu A = 0.029$$

$$i_{in} = \frac{V_{in}}{R_s} = 0.04 \mu A \quad 0.73 \mu A \times 0.04 =$$

$$\Rightarrow R_M = \frac{V_{out}}{i_{in}} = \frac{-150 \text{ mV}}{0.04 \mu A} = -3750 \times 10^{-3}$$



$$R_M = -3.75 \Omega = -3.75 \Omega$$

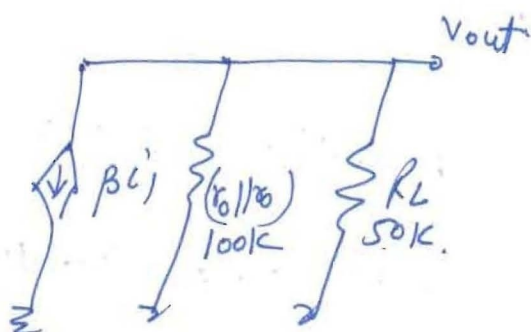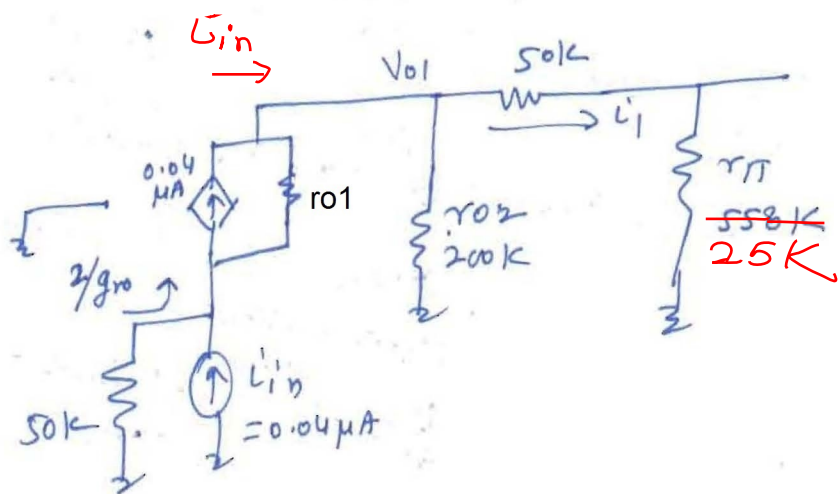

(2)

$$R_{in} i_{in} = -3.75 i_{in}$$


Q 3

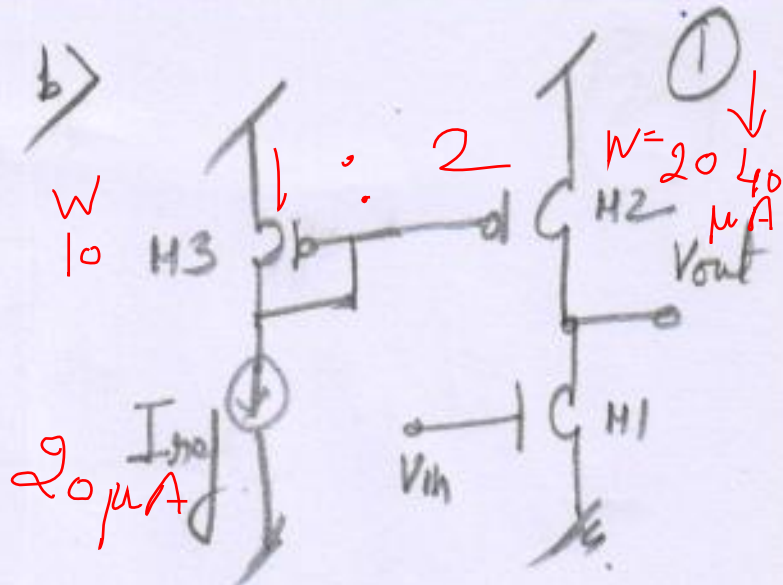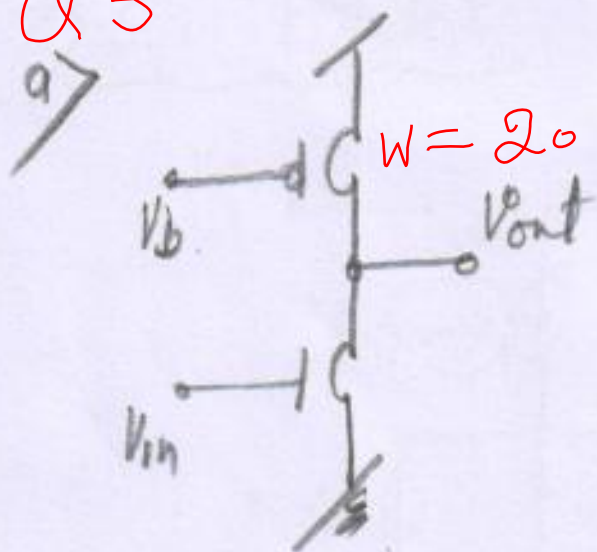

$$I_{out} = \frac{W_2}{W_3} \times I_{ref}$$

$$W_3 = 20 \mu m \times \frac{20 \mu A}{40 \mu A}$$

$$W_3 = 10 \mu m$$

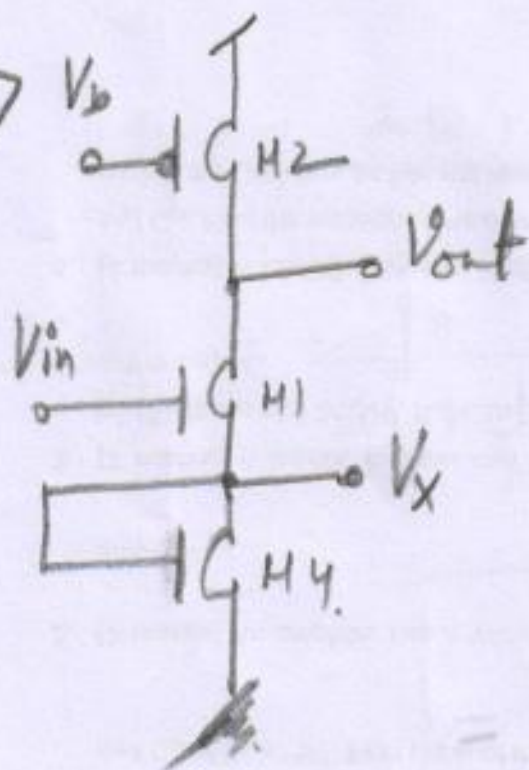

@ Node Vout

$$d) A_v = \frac{-g_m R_D}{1 + g_m R_S}$$

$$R_D = r_{o2}$$

$$R_S = \frac{1}{g_{m4}}$$

$$-g_m = \frac{2I_D}{V_{ov}} = \frac{40 \mu A}{0.2} = 200 \mu A/V$$

$$-r_o = \frac{1}{\lambda I_D} = \frac{1}{0.2 \times 40 \mu A} = 250 k\Omega$$

$$g_{m4} = 200 \mu A/V$$


$$-1/g_{m4} = \frac{1}{200 \mu A} \approx 5 k\Omega$$

$$A_v = \frac{200 \times 10^{-6} \times 250 \times 10^3}{1 + 200 \times 10^{-6} \times 5 \times 10^3}$$

$$A_v = \frac{250}{5} \approx 50$$

d) Gain at node X

(2)

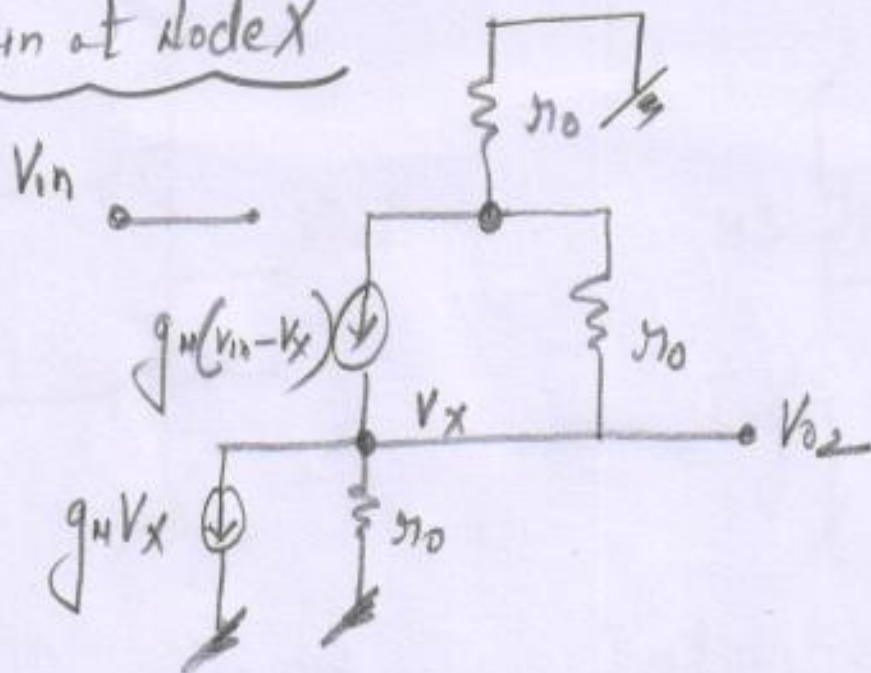

$$g_m(V_{in} - V_x) = g_m V_x + \frac{V_x}{r_o} + \frac{V_x}{2r_o}$$

$$g_m V_{in} = 2g_m V_x + \frac{V_x}{r_o} + \frac{V_x}{2r_o} = V_x \left[2g_m + \frac{1}{r_o} + \frac{1}{2r_o} \right]$$

$$\frac{V_{o2}}{V_{in}} = \frac{V_x}{V_{in}} = \frac{g_m}{2g_m + \frac{1}{r_o} + \frac{1}{2r_o}} \approx \frac{g_m}{2g_m} = \frac{1}{2}$$

$$\boxed{\frac{V_{o2}}{V_{in}} = \frac{1}{2}}$$

f) No effect on GTR.


Q4

a) $V_o = -g_m V_i (r_o \parallel R_L) \Rightarrow$ Voltage gain: $\frac{V_o}{V_i} = -g_m (r_o \parallel R_L)$ [4]

given $r_o = R_L = \frac{1}{g_m} \Rightarrow r_o \parallel R_L = \frac{1}{2g_m}$

$\left\{ \frac{V_o}{V_i} = -g_m \cdot \frac{1}{2g_m} = -\frac{1}{2} \right.$

gain in dB = $20 \log \left| \frac{V_o}{V_{in}} \right| = 20 \log \frac{1}{2}$
 $= -6.02 \text{ dB}$ [4]

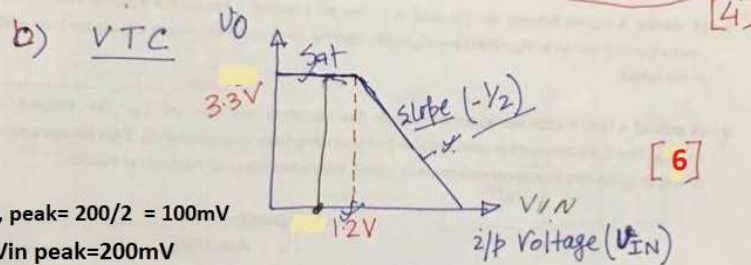

$V_o, \text{ peak} = 200/2 = 100 \text{ mV}$

$V_{in} \text{ peak} = 200 \text{ mV}$

c) $P_L = \frac{V_{o, \text{rms}}^2}{R_L} = \frac{(0.1/\sqrt{2})^2}{1000} = 0.005 \text{ mW}$

$P_{dc} = 3.3 \times 1 \text{ mW} = 3.3 \text{ mW}$

Power efficiency (η) = $\frac{0.005}{3.3} \times 100 \%$

$= \underline{\underline{0.152 \pm 0.001 \%}}$ [5]

Part B (OB)

① Solⁿ

$$A_{OL} = 100 \text{ dB}$$

$$A_{OL} = 10^5$$

$$A_{CL} = 40 \text{ dB}$$

$$A_{CL} = 10^2$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL} \beta}$$

$$\frac{A_{OL} \beta}{\beta} = \frac{10^3}{10^{-2}}$$

$$\text{So } \beta \text{ (feedback factor)} = \frac{10^{-2}}{10^3} \rightarrow \textcircled{2}$$

$$A_{OL} \beta \text{ (Loop gain)} = \frac{10^3}{10^3} \rightarrow \textcircled{2}$$

Shunt $\rightarrow R_{if} = \frac{R_{in}}{(1 + A_{OL} \beta)} = \frac{100 \Omega}{10^3} \text{ (shunt Resistance)}$ $\downarrow$ $\textcircled{2}$

$$R_{in} = 100 \text{ k}\Omega$$


$$R_{out} = 0.1 \text{ k}\Omega$$

Series $\rightarrow R_{of} = R_{out} (1 + A_{OL} \beta) = 0.1 \text{ M}\Omega = 100 \text{ k}\Omega$ $\textcircled{2}$

3-dB Bandwidth = BW increases by $(1 + A_{OL} \beta)$

$$BW_i = 1 \text{ K rad/sec} (1 + A_{OL} \beta) = 10^6 \text{ rad/sec}$$
 $\textcircled{2}$

②

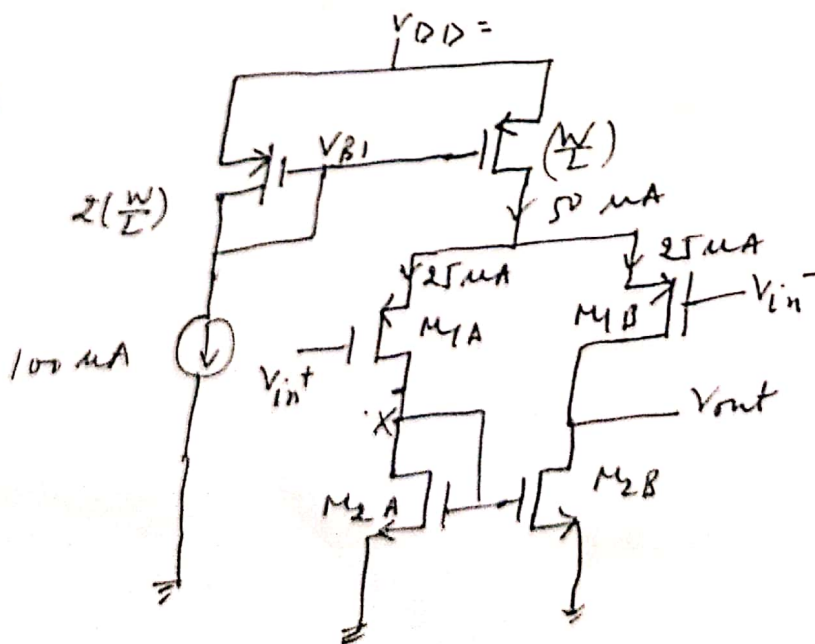

$$V_{ov} = 0.25 \text{ V}$$

$$V_A|_{n,p} = 10 \text{ V}$$

$$V_{TH}|_{n,p} = 0.65 \text{ V}$$

Solⁿ: from current mirror property:
current passing through M_A & M_B will be $25 \mu A$ respectively.

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2 \times 25 \times 10^{-6}}{0.25} = 0.2 \text{ mA/V}$$

$$r_{o|n,p} = \frac{V_A}{I_D} = \frac{100 \text{ V}}{25 \times 10^{-6}} = 4 \text{ M}\Omega$$

a) Differential gain (A_{DM}) = $-g_{m_p} (r_{o|n} || r_{o|p})$
 $= -0.2 \times 10^{-3} [4 || 4] \times 10^6$
 $[A_{DM} = -400 \text{ V/V}] - (2)$

b) $V_{out}(\text{Swing}) -$

$$V_{out}(\text{max}) = V_{DD} - 2V_{ov} = 2.5 - 0.5 = 2 \text{ V}$$

$$V_{out}(\text{min}) = V_{ov} = 0.25 \text{ V}$$

$$\therefore V_{out}(\text{Swing}) = 2 - 0.25 = 1.75 \text{ V} - (2)$$

c) Value of I_{CM} & $V_{out}(\text{DC}) = V_{TH} + V_{ov} = 0.90 \text{ V}$

$$V_{in}(\text{lower limit}) = V_{out}(\text{DC}) + V_{TH} = 0.9 + 0.65 = 1.55 \text{ V}$$

$$V_{in}(\text{Upper limit}) = V_{DD} - V_{ov} + V_{GS|p} = 2.5 + 0.90 = 3.40 \text{ V}$$


(3)

d) $V_{out} = V_{out}(\text{DC}) - 0.1 \sin \omega t \times 400 \text{ mV}$

$$V_{out} = (900 - 40 \sin \omega t) \text{ mV} - (3)$$

e)

$$\therefore V_p|_{\text{max}} = \frac{0.65}{A_{DM}} = \frac{0.65}{400} = 1.625 \text{ mV}$$

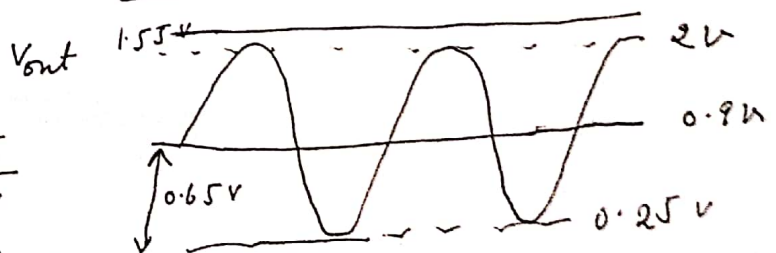

(3)

f) Input offset voltage

$$= \frac{V_{ov}}{2} \left(\frac{\Delta(w/L)}{w/L} \right)$$

$$\frac{\Delta(w/L)}{w/L} = 5\%$$

$$= \frac{0.25}{2} \times 0.05$$

$$= \underline{6.25 \text{ mV}} \rightarrow \textcircled{2}$$

g) Dominant pole f

$$C_x = 200 \text{ fF}$$

$$C_{load} = 2 \text{ pF}$$

$$\frac{1}{R_{out} C_{load}} = \frac{1}{2 \text{ M}\Omega \times 2 \text{ pF}}$$

$$= 0.25 \times 10^6$$

$$\omega_{\text{dominant pole}} = \underline{250 \text{ K rad/s}} \rightarrow \textcircled{2}$$

$$\begin{aligned} \text{Mirror pole} &= \frac{f_{mtn}}{\text{frequency}} = \frac{0.2 \times 10^{-3}}{200 \times 10^{-15}} = 0.1 \times 10^{10} \text{ rad/s} \\ &= \underline{1 \text{ G rad/sec}} \end{aligned}$$

↑ $\textcircled{2}$

Part-B OB

$$\frac{Y(s)}{X(s)} = \frac{20 \times 20 \left(\frac{j\omega}{20} + 1 \right)}{2 \times 10 \left[\frac{j\omega}{2} + 1 \right] \left[\frac{j\omega}{10} + 1 \right]} = \frac{20 \left(\frac{j\omega}{20} + 1 \right)}{\left(\frac{j\omega}{2} + 1 \right) \left(\frac{j\omega}{10} + 1 \right)}$$

Unity Gain frequency: $\left| \frac{Y(j\omega)}{X(j\omega)} \right| = 1$

$$20 \sqrt{\left(\frac{\omega}{20} \right)^2 + 1} = \sqrt{\left(\frac{\omega}{2} \right)^2 + 1} \sqrt{\left(\frac{\omega}{10} \right)^2 + 1}$$

$$400 \left[\frac{\omega^2}{400} + 1 \right] = \left(\frac{\omega^2}{400} + \frac{104\omega^2}{400} + 1 \right)$$

$$\frac{\omega^2}{400} + \frac{(104-400)\omega^2}{400} - 399 = 0$$

$$\omega^2 + -296\omega^2 - 399 \times 400 = 0$$

$$\omega^2 = 574.03 \text{ (or)} -278.03$$

$$\omega = 24 \text{ rad/sec} \quad \text{Gain crossover freq.}$$

Phase @ $\omega_{\text{cxf}} \Rightarrow \tan^{-1}\left(\frac{\omega}{20}\right) - \tan^{-1}\left(\frac{\omega}{2}\right) - \tan^{-1}\left(\frac{\omega}{10}\right)$

$$= -102.4^\circ \text{ is the phase @ } \omega_{\text{cxf}}$$

$$\text{Phase Margin} = 180^\circ - 102.4^\circ = 77.5^\circ$$

The system has one pole (20 rad/sec) and two zeros one each at 2 rad/sec and 10 rad/sec. Initial phase is 0° ($\omega=0$). Therefore the system will never see a phase of 180° . $\therefore$ phase crossover frequency is undefined
Gain Margin is infinity.

3 dB Bandwidth:-

$$2 \left[\frac{\omega^2}{400} + 1 \right] = \left[\frac{\omega^2}{4} + 1 \right] \left[\frac{\omega^2}{100} + 1 \right]$$

$$2\omega^2 + 800 = \omega^4 + 104\omega^2 + 400$$

$$\omega^4 + 102\omega^2 - 400 = 0 \quad \omega^2 = 3.78 \text{ (or)} -105$$

$$\text{3dB Bandwidth} = 1.94 \text{ rad/sec}$$

Since the pole at 10 rad/sec and zero at 20 rad/sec are two octaves above the pole at 2 rad/sec we can say the pole at 2 rad/sec is the dominant pole.

$$\therefore \omega_{\text{dB}} = 2 \text{ rad/sec}$$

Gain of the CSA (M1-M2) $\therefore -\beta_{\text{m}} (X_{01} \parallel X_{02})$

$$= -0.2 (400k \parallel 600k) \text{ mA/V}$$

$$A_v = -48$$

This is also the gain of stage-2 CSA (M3-M4).

Cap. at node P $\therefore C_{gs1} + C_{gd1}(1+A_v)$

$$= 100 \text{ fF} + 50(1+48) \text{ fF}$$

$$= 2.55 \text{ pF}$$

Cap. at node-X:-

$$[C_{gd1} + C_{db1}] + [C_{db2}] + [C_{gs3} + C_{gd3}(1+A_v)]$$

from M1 from M2 from M3

$$= 70\text{fF} + 80\text{fF} + 100\text{fF} + 50\text{fF}(1+4.8)$$

$$= \underline{\underline{2.7\text{pF}}}$$

OTC Method

When we combine all the intrinsic cap. that can be added.

$$C_1 = C_{gs1} ; 100\text{fF}$$

$$C_2 = C_{gd1} ; 50\text{fF}$$


$$C_3 = C_{db1} + C_{gd2} + C_{db2} + C_{gs3} + C_{gd3}(1+A_v) = 2.65\text{pF}$$

Therefore we will calculate three time constants

$$R_1 = R_{sig} = (R_{gs}) = 100\text{k}\Omega$$

$$R_3 = R_L' = X_{01} || X_{03} = 240\text{k}\Omega$$
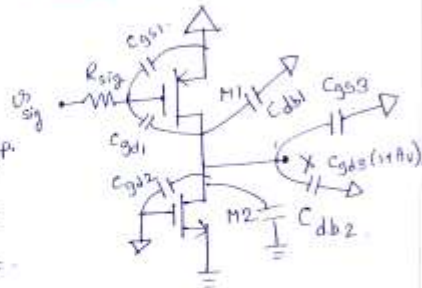
$$R_2 = R_{gd} = R_{sig} (1 + g_m R_L') + R_L' = 5.14\text{M}\Omega$$



$$T_1 = R_1 C_1 = 10\text{nS}$$

$$T_2 = R_2 C_2 = 13.621\mu\text{S}$$

$$T_3 = 12\text{nS}$$

$$T_H = T_1 + T_2 + T_3$$

$$= 13.643\mu\text{S}$$

$$\omega_H = 73.29\text{Krad/sec} \quad (11.7\text{KHz})$$

Resistance at node-Q:- $(X_{02} || X_{04}) = 240\text{k}\Omega$

$$\omega_G = (240\text{k}\Omega \times C_{Load}')^{-1} = 500\text{Krad/sec}$$

$$C_{Load}' = 8.3\text{pF}$$

intrinsic cap. connected to node-Q:-

$$C_{db4} + C_{gd4} + C_{gd3} + C_{db3} = 150\text{fF} \text{ (too small)}$$

$$\therefore C_{Load} \approx \underline{\underline{8.3\text{pF}}}$$

$$CHFR = \frac{A_{0H}}{A_{cH}} \quad \text{Given } A_{0H} = \frac{G_{M1}}{(1 + \frac{j\omega}{P_1})} \quad P_1 = 40\text{Mrad/sec}$$

$$\text{We know } A_{cH} \text{ has a zero at } \omega_z = (R_{gs} C_{gs})^{-1} = 100\text{Mrad/sec}$$

$$CHFR = \frac{K(\text{some constants})}{(1 + \frac{j\omega}{40})(1 + \frac{j\omega}{100})} \quad \text{[in Mrad/sec]}$$

$$\omega_{3dB} = \underline{\underline{95.28\text{Mrad/sec}}}$$

Prepared by

Dr. K. Babu Ravi Teja

Assistant Professor, Department of EEE

BITS Pilani, Pilani Campus

Mail: baburaviteja.k@pilani.bits-pilani.ac.in

